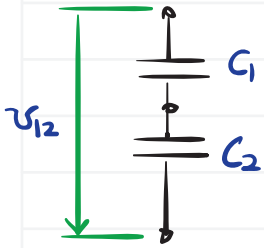


$$\begin{aligned} E &= \int_0^t VI \, dt \\ &= \int_0^t vC \frac{dv}{dt} dt \\ &= C \int_{v(0)}^{v_f} v \, dv \\ &= \frac{1}{2} C (v_f^2 - v(0)^2) \\ &= \frac{1}{2} C v_f^2 \end{aligned}$$



$$\text{KCL: } i_{c1} = i_{c2} = i$$

$$\text{Elemental: } i_{c1} = C_1 \frac{dv_{c1}}{dt} \quad i_{c2} = C_2 \frac{dv_{c2}}{dt}$$

$$\Rightarrow v_{c1} = \frac{1}{C_1} \int_0^t i \, dt \quad v_{c2} = \frac{1}{C_2} \int_0^t i \, dt$$

$$\begin{aligned} \text{KVL: } v_{12} &= v_{c1} + v_{c2} \\ &= \frac{1}{C_1} \int_0^t i \, dt + \frac{1}{C_2} \int_0^t i \, dt \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int_0^t i \, dt \end{aligned}$$

$$\Rightarrow \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} v_{12} = \int_0^t i \, dt$$

$$\Rightarrow \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \frac{dv_{12}}{dt} = i$$


This is in the form of an elemental eq. for a capacitor with capacitance

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \quad \text{QED}$$

From Assignment #3

1/

For the circuit diagram below, perform a complete circuit analysis to solve for $v_o(t)$ if $V_s(t) = A \sin \omega t$, where $A \in \mathbb{R}$ is a given amplitude and $\omega \in \mathbb{R}$ is a given angular frequency. Let $i_L(t)|_{t=0} = 0$ be the initial inductor current. Hint: you will need to solve a differential equation for $i_L(t)$.

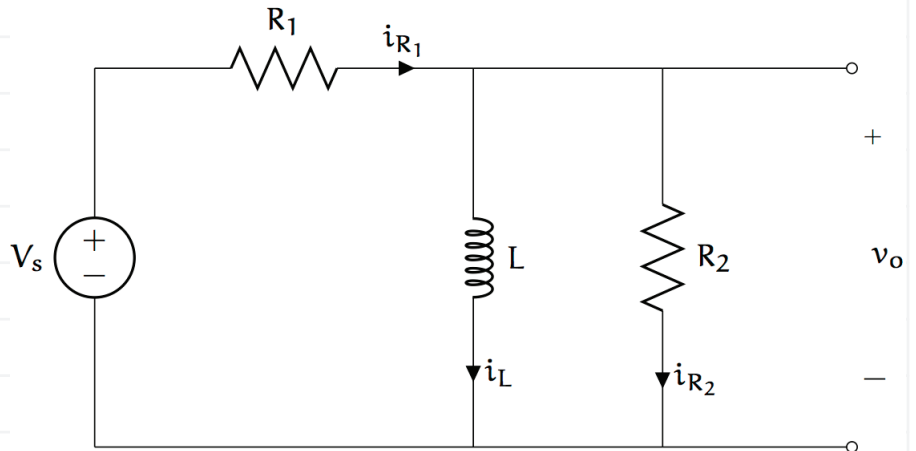

1. Signs. Already given

2. El. eq. $v_{R_1} = i_{R_1} R_1$ $v_{R_2} = i_{R_2} R_2$ $v_L = L \frac{di_L}{dt}$

3. KCL. $i_{R_1} = i_L + i_{R_2}$

4. KVL. $V_s = v_{R_1} + v_L$ $v_L = v_{R_2}$ $v_o = v_{R_2}$

5. Algebra.

$$\begin{aligned} \frac{di_L}{dt} &= \frac{1}{L} v_L = \frac{1}{L} v_{R_2} = \frac{R_2}{L} i_{R_2} = \frac{R_2}{L} (i_{R_1} - i_L) \\ &= \frac{R_2}{L} \left(\frac{v_{R_1}}{R_1} - i_L \right) \\ &= \frac{R_2}{L} \left(\frac{1}{R_1} (V_s - v_L) - i_L \right) \\ &= \frac{R_2}{L} \left(\frac{1}{R_1} \left(V_s - L \frac{di_L}{dt} \right) - i_L \right) \Rightarrow \end{aligned}$$

$$\underbrace{\left(\frac{L}{R_2} + \frac{L}{R_1} \right)}_{\tau} \frac{di_L}{dt} + i_L = \frac{1}{R_1} V_s .$$

6. DE. Solve DE for $i_L(t)$. Then $v_o(t) = v_L(t) = L \frac{di_L}{dt}$.