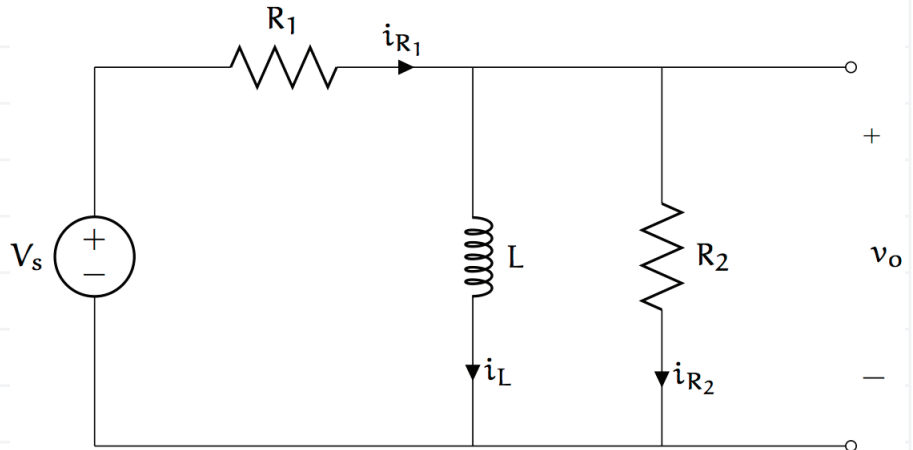


Special Problem #3. For the circuit diagram below, solve for the *steady state*  $v_o(t)$  if  $V_s(t) = A \sin \omega t$ , where  $A \in \mathbb{R}$  is a given amplitude and  $\omega \in \mathbb{R}$  is a given angular frequency. Use impedances!



1. Signs. Already given

2. El. eq.  $v_{R_1} = i_{R_1} R_1$      $v_{R_2} = i_{R_2} R_2$      $v_L = i_L Z_L$   
 ( $Z_L = j\omega L$ )

3. KCL.  $i_{R_1} = i_L + i_{R_2}$

4. KVL.  $V_s = v_{R_1} + v_L$      $v_L = v_{R_2}$      $v_o = v_{R_2}$

5. Algebra. We could use the above equations, but we will take a shortcut. The generalized voltage divider can be applied if we combine the impedances of  $L$  and  $R_2$ :

$$Z_o = \frac{R_2 Z_L}{R_2 + Z_L} = \frac{j\omega R_2 L}{R_2 + j\omega L}$$

The generalized voltage divider for  is

$$v_o = \frac{Z_o}{Z_o + R_1} V_s$$

This is equivalent to the lengthier analysis that proceeds from the elemental eq's, KCL, + KVL.

All that remains is complex algebra:

2/

$$\begin{aligned}v_o &= \frac{j\omega R_2 L}{R_2 + j\omega L} \frac{j\omega R_2 L}{R_2 + j\omega L} + R_1 V_s \\&= \frac{j\omega R_2 L}{j\omega R_2 L + R_1(R_2 + j\omega L)} V_s \\&= \frac{j\omega R_2 L}{R_1 R_2 + j\omega L(R_1 + R_2)} V_s \\&= \frac{R_1 R_2 - j\omega L(R_1 + R_2)}{R_1 R_2 - j\omega L(R_1 + R_2)} \cdot \frac{j\omega R_2 L}{R_1 R_2 + j\omega L(R_1 + R_2)} V_s \\&= \frac{R_2(R_1 + R_2)(\omega L)^2 + j\omega R_1 R_2^2 L}{(R_1 R_2)^2 + (\omega L(R_1 + R_2))^2} V_s \\&= \frac{((R_2(R_1 + R_2)(\omega L)^2)^2 + (\omega R_1 R_2^2 L)^2)^{1/2}}{(R_1 R_2)^2 + (\omega L(R_1 + R_2))^2} e^{j\psi} V_s, \\&\quad \underbrace{\hspace{15em}}_{|Z_e|}\end{aligned}$$

where  $\psi = \arctan \frac{\omega R_1 R_2^2 L}{R_2(R_1 + R_2)(\omega L)^2} = \arctan \frac{R_1 R_2}{(R_1 + R_2)\omega L}$ .

Insert  $V_s = A \sin \omega t = A \cos(\omega t - \pi/2) = A e^{j\pi/2}$  :

$$\begin{aligned}v_o &= |Z_e| e^{j\psi} (A e^{-j\pi/2}) \\&= A |Z_e| e^{j(\psi - \pi/2)} \\&= A |Z_e| \cos(\omega t + \psi - \pi/2).\end{aligned}$$