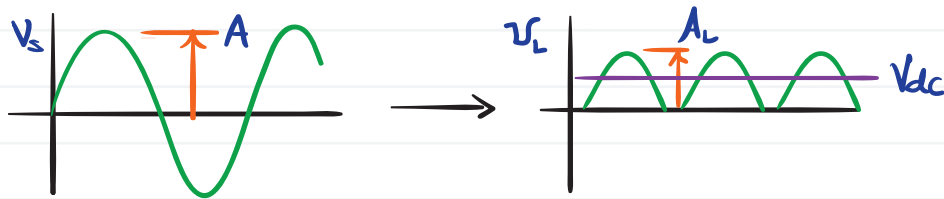


DC voltage

Source delivers amplitude A across three drops (two diodes and the load/capacitor). Considering amplitudes only,

$$A = 0.6 + 0.6 + A_L \Rightarrow A_L = A - 1.2 .$$



It is roughly true that

$$V_{dc} = \frac{1}{T/2} \int_0^{T/2} A_L \sin \omega t \, dt$$

$$= \frac{2}{\pi} \cdot A_L .$$

If we want $V_{dc} = 10 \text{ V}$, $A_L = \frac{\pi}{2} (10) = 15.7 \text{ V}$. Therefore,

$$A = A_L + 1.2 = 16.9 \text{ V} .$$

Ripple voltage

We know $\Delta V = \frac{i_L}{2fC}$. We require $\Delta V < 0.1 V_{pp}$:

$$\frac{i_L}{2fC} < 0.1 \Rightarrow$$

ripple freq. \Rightarrow 2 input freq.

$$C > \frac{5 i_L}{f} = \frac{5 (100^{-3})}{(2 \cdot 60)} = 417 \mu\text{F} .$$

assume 60Hz line

$$\Rightarrow C > 417 \mu\text{F} .$$