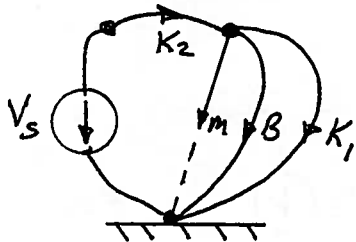


5-2

PROBLEM S.2

(a) SYSTEM a



(b) ORDER = 3

ST. VAR.:  $v_m, F_{K_1}, F_{K_2}$

(c)  $\frac{dv_m}{dt} = \frac{1}{m} [F_m]$

$\frac{dF_{K_1}}{dt} = K_1 v_{K_1}$

$\frac{dF_{K_2}}{dt} = K_2 v_{K_2}$

$F_B = B v_B$

$F_m = F_{K_2} - F_B - F_{K_1}$

$v_{K_1} = v_m$

$v_{K_2} = v_s - v_m$

$v_B = v_m$


The 3 st. EQ.

$\frac{dv_m}{dt} = \frac{1}{m} [F_{K_2} - F_{K_1} - Bv_m]$

$\frac{dF_{K_1}}{dt} = K_1 v_m$

$\frac{dF_{K_2}}{dt} = K_2 [v_s - v_m]$

SYSTEM b

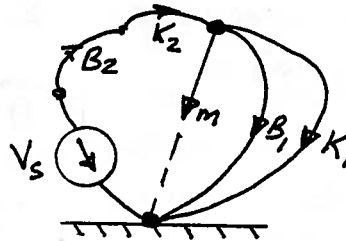

ORDER = 3

ST. VAR.:  $v_m, F_{K_1}, F_{K_2}$

$\frac{dv_m}{dt} = \frac{1}{m} [F_m]$

$\frac{dF_{K_1}}{dt} = K_1 v_{K_1}$

$\frac{dF_{K_2}}{dt} = K_2 v_{K_2}$

$F_{B_1} = B_1 v_{B_1}$

$v_{B_2} = \frac{1}{B_2} F_{B_2}$

$F_m = F_{K_2} - F_{B_1} - F_{K_1}$

$v_{K_1} = v_m$

$v_{K_2} = v_s - v_{B_2} - v_m$

$v_{B_1} = v_m$

$F_{B_2} = F_{K_2}$

The 3 st. EQ.

$\frac{dv_m}{dt} = \frac{1}{m} [F_{K_2} - B_1 v_m - F_{K_1}]$

$\frac{dF_{K_1}}{dt} = K_1 [v_m]$

$\frac{dF_{K_2}}{dt} = K_2 [v_s - \frac{F_{K_2}}{B_2} - v_m]$

## PROBLEM 5.2 CONTINUED

$$\frac{d}{dt} \begin{bmatrix} v_m \\ F_{K_1} \\ F_{K_2} \end{bmatrix} =$$

$$\begin{bmatrix} -\frac{B_1}{M} & -\frac{1}{M} & \frac{1}{M} \\ K_1 & 0 & 0 \\ -K_2 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} v_m \\ F_{K_1} \\ F_{K_2} \end{bmatrix}$$

$$+ \begin{bmatrix} 0 \\ 0 \\ K_2 \end{bmatrix} V_s$$

$$\frac{d}{dt} \begin{bmatrix} v_m \\ F_{K_1} \\ F_{K_2} \end{bmatrix} =$$

$$\begin{bmatrix} -\frac{B_1}{M} & -\frac{1}{M} & \frac{1}{M} \\ K_1 & 0 & 0 \\ -K_2 & 0 & -\frac{K_2}{B_2} \end{bmatrix} \cdot \begin{bmatrix} v_m \\ F_{K_1} \\ F_{K_2} \end{bmatrix}$$

$$+ \begin{bmatrix} 0 \\ 0 \\ K_2 \end{bmatrix} V_s$$

(d)

$$\text{OUTPUT} = y = v_m$$


$$y = [1 \ 0 \ 0] \begin{bmatrix} v_m \\ F_{K_1} \\ F_{K_2} \end{bmatrix}$$

$$\text{OUTPUT} = y = v_m$$

$$y = [1 \ 0 \ 0] \begin{bmatrix} v_m \\ F_{K_1} \\ F_{K_2} \end{bmatrix}$$

5-8

PROBLEM 5.6

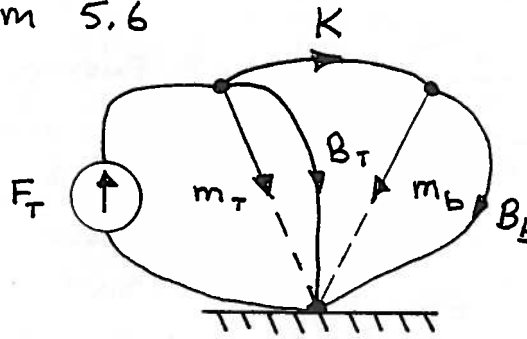

STATE VAR.

$$v_{m_T}, v_{m_b}, F_K$$

( )<sub>T</sub> = Tug Boat

( )<sub>b</sub> = barge

K: elastic cable

$$\frac{dv_{m_T}}{dt} = \frac{1}{m_T} F_{m_T} \quad \left| \quad F_{m_T} = F_T - F_K - F_{B_T}$$

$$\frac{dv_{m_b}}{dt} = \frac{1}{m_b} F_{m_b} \quad \left| \quad F_{m_b} = F_K - F_{B_b}$$

$$\frac{dF_K}{dt} = K v_K \quad \left| \quad v_K = v_{m_T} - v_{m_b}$$

$$F_{B_T} = B_T v_{B_T} \quad \left| \quad v_{B_T} = v_{m_T}$$

$$F_{B_b} = B_b v_{B_b} \quad \left| \quad v_{B_b} = v_{m_b}$$

$$\frac{dv_{m_T}}{dt} = \frac{1}{m_T} [ F_T - F_K - B_T v_{m_T} ]$$

$$\frac{dv_{m_b}}{dt} = \frac{1}{m_b} [ F_K - B_b v_{m_b} ]$$

$$\frac{dF_K}{dt} = K [ v_{m_T} - v_{m_b} ]$$


$$\frac{d}{dt} \begin{bmatrix} v_{m_T} \\ v_{m_b} \\ F_K \end{bmatrix} = \begin{bmatrix} -B_T/m_T & 0 & -1/m_T \\ 0 & -B_b/m_b & 1/m_b \\ K & -K & 0 \end{bmatrix} \cdot \begin{bmatrix} v_{m_T} \\ v_{m_b} \\ F_K \end{bmatrix} + \begin{bmatrix} 1/m_T \\ 0 \\ 0 \end{bmatrix} F_T$$

$$y = v_{m_b} = [ 0 \ 1 \ 0 ] \begin{bmatrix} v_{m_T} \\ v_{m_b} \\ F_K \end{bmatrix}$$

PROBLEM 5.8

SYSTEM (a)

(a)

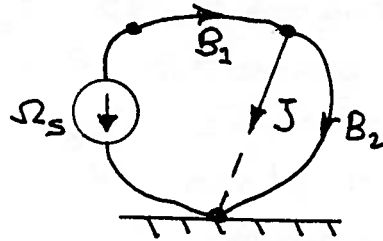

(b)

$$\frac{d\Omega_J}{dt} = \frac{1}{J} T_J \quad \Bigg| \quad T_J = T_{B_1} - T_{B_2}$$

$$T_{B_1} = B_1 \Omega_{B_1} \quad \Bigg| \quad \Omega_{B_1} = \Omega_s - \Omega_J$$


$$T_{B_2} = B_2 \Omega_{B_2} \quad \Bigg| \quad \Omega_{B_2} = \Omega_J$$

$$\frac{d\Omega_J}{dt} = \left[ \frac{-(B_1 + B_2)}{J} \right] \Omega_J + \left[ \frac{B_1}{J} \right] \Omega_s$$

(c) OUTPUT =  $y = [1] [\Omega_J]$

SYSTEM (b)

(a)

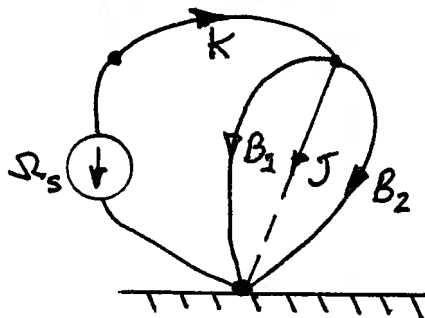

STATE VAR.  
 $\Omega_J, T_K$

## PROBLEM 5.8 CONTINUED

$$\begin{array}{l|l}
 \text{(b)} \quad \frac{d\Omega_J}{dt} = \frac{1}{J} T_J & T_J = T_K - T_{B_1} - T_{B_2} \\
 \frac{dT_K}{dt} = K \Omega_K & \Omega_K = \Omega_S - \Omega_J \\
 T_{B_1} = B_1 \Omega_{B_1} & \Omega_{B_1} = \Omega_J \\
 T_{B_2} = B_2 \Omega_{B_2} & \Omega_{B_2} = \Omega_J
 \end{array}$$

$$\frac{d\Omega_J}{dt} = \frac{1}{J} (B_1 + B_2) \Omega_J + \frac{1}{J} T_K$$

$$\frac{dT_K}{dt} = -K \Omega_J + K \Omega_S$$


$$\frac{d}{dt} \begin{bmatrix} \Omega_J \\ T_K \end{bmatrix} = \begin{bmatrix} \frac{-(B_1 + B_2)}{J} & \frac{1}{J} \\ -K & 0 \end{bmatrix} \cdot \begin{bmatrix} \Omega_J \\ T_K \end{bmatrix} + \begin{bmatrix} 0 \\ K \end{bmatrix} \Omega_S$$

$$\text{(c)} \quad y = [1 \ 0] \begin{bmatrix} \Omega_J \\ T_K \end{bmatrix}$$

S-14

PROBLEM S.11

SYSTEM (a)

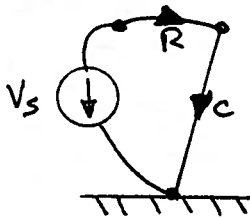

$$\frac{dv_c}{dt} = \frac{1}{C} i_c$$


$$i_c = i_R$$

$$i_R = v_R/R$$

$$v_R = v_s - v_c$$

$$\frac{dv_c}{dt} = \left[ \frac{-1}{RC} \right] v_c + \left[ \frac{1}{RC} \right] v_s$$

SYSTEM (b)

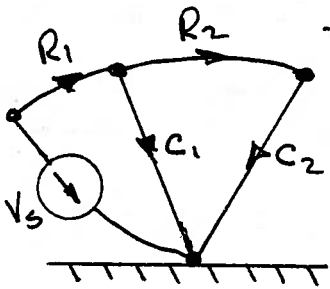

$$\frac{dv_{c1}}{dt} = \frac{1}{C_1} i_{c1}$$

$$i_{c1} = i_{R1} - i_{R2}$$

$$\frac{dv_{c2}}{dt} = \frac{1}{C_2} i_{c2}$$

$$i_{c2} = i_{R2}$$

$$i_{R1} = v_{R1}/R_1$$

$$v_{R1} = v_s - v_{c1}$$



$$i_{R2} = v_{R2}/R_2$$

$$v_{R2} = v_{c1} - v_{c2}$$

$$\frac{d}{dt} \begin{bmatrix} v_{c1} \\ v_{c2} \end{bmatrix} = \begin{bmatrix} (-1/R_1 C_1 + 1/R_2 C_1) & 1/R_2 C_1 \\ 1/C_2 R_2 & -1/R_2 C_2 \end{bmatrix} \cdot \begin{bmatrix} v_{c1} \\ v_{c2} \end{bmatrix} + \begin{bmatrix} 1/R_1 C_1 \\ 0 \end{bmatrix} v_s$$

$$y = v_{c2} = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} v_{c1} \\ v_{c2} \end{bmatrix}$$

## PROBLEM 5.12

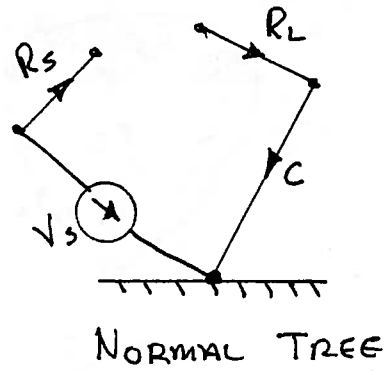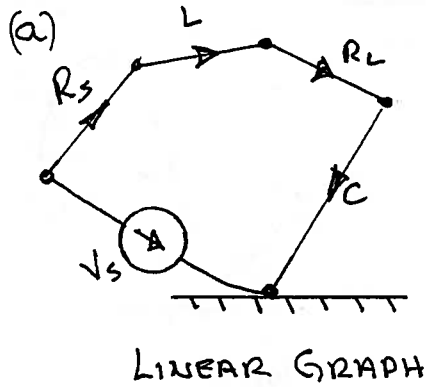SYSTEM (a)

(b)

$$\frac{dv_c}{dt} = \frac{1}{C} i_c$$

$$\frac{di_L}{dt} = \frac{1}{L} v_L$$

$$v_{R_s} = R_s i_{R_s}$$

$$v_{R_L} = R_L i_{R_L}$$

$$i_c = i_L$$

$$v_L = v_s - v_{R_s} - v_{R_L} - v_c$$

$$i_{R_s} = i_L$$

$$i_{R_L} = i_L$$

$$\frac{d}{dt} \begin{bmatrix} v_c \\ i_L \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/L & -(R_s + R_L)/L \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} v_s$$

(c)


$$y = v_{out} = v_c + v_{R_L} + v_L = v_s - v_{R_s} = v_s - R_s i_L$$

$$y = \begin{bmatrix} 0 & -R_s \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix} + \begin{bmatrix} 1 \end{bmatrix} [v_s]$$


S-16

PROBLEM 5.12 CONTINUED  
SYSTEM (b)

(a)

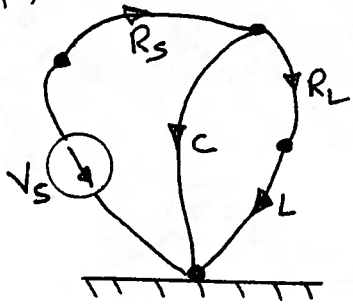

LINEAR GRAPH

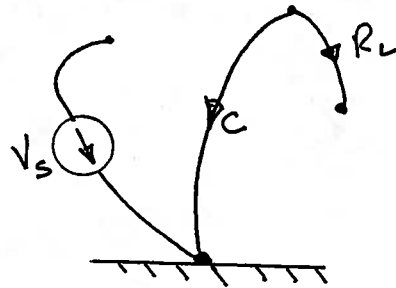

NORMAL TREE

(b)

$$\begin{array}{l}
 \frac{dv_c}{dt} = \frac{1}{C} i_c \\
 \frac{di_L}{dt} = \frac{1}{L} v_L \\
 v_{R_L} = R_L i_{R_L} \\
 i_{R_S} = \frac{1}{R_S} v_{R_S}
 \end{array}
 \quad \left\| \right.
 \quad
 \begin{array}{l}
 i_c = i_{R_S} - i_L \\
 v_L = v_c - v_{R_L} \\
 i_{R_L} = i_L \\
 v_{R_S} = v_s - v_c
 \end{array}$$


$$\frac{d}{dt} \begin{bmatrix} v_c \\ i_L \end{bmatrix} = \begin{bmatrix} -1/C R_S & -1/C \\ 1/L & -R_L/L \end{bmatrix} \cdot \begin{bmatrix} v_c \\ i_L \end{bmatrix} + \begin{bmatrix} 1/C R_S \\ 0 \end{bmatrix} v_s$$

(c) OUTPUT =  $y = v_c$


$$y = [1 \ 0] \begin{bmatrix} v_c \\ i_L \end{bmatrix}$$



## PROBLEM 5.13

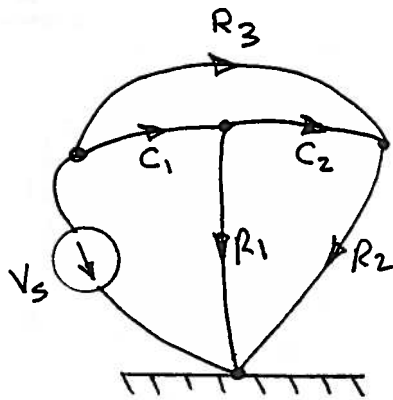

LINEAR GRAPH

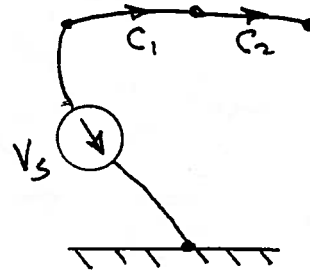

NORMAL TREE

$$\frac{dV_{C_1}}{dt} = \frac{1}{C_1} i_{C_1}$$

$$\frac{dV_{C_2}}{dt} = \frac{1}{C_2} i_{C_2}$$

$$i_{R_1} = \frac{1}{R_1} V_{R_1}$$

$$i_{R_2} = \frac{1}{R_2} V_{R_2}$$

$$i_{R_3} = \frac{1}{R_3} V_{R_3}$$

$$i_{C_1} = i_{R_1} + i_{R_2} - i_{R_3}$$

$$i_{C_2} = i_{R_2} - i_{R_3}$$

$$V_{R_1} = V_s - V_{C_1}$$

$$V_{R_2} = V_s - V_{C_1} - V_{C_2}$$

$$V_{R_3} = V_{C_1} + V_{C_2}$$

$$\frac{dV_{C_1}}{dt} = \frac{1}{C_1} \left[ \frac{V_s - V_{C_1}}{R_1} + \frac{V_s - V_{C_1} - V_{C_2}}{R_2} - \frac{V_{C_1} + V_{C_2}}{R_3} \right]$$

$$\frac{dV_{C_2}}{dt} = \frac{1}{C_2} \left[ \frac{V_s - V_{C_1} - V_{C_2}}{R_2} - \frac{V_{C_1} + V_{C_2}}{R_3} \right]$$

$$\frac{d}{dt} \begin{bmatrix} V_{C_1} \\ V_{C_2} \end{bmatrix} = \begin{bmatrix} \frac{1}{C_1} \left( -\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_3} \right) & -\frac{1}{C_1} \left( \frac{1}{R_2} + \frac{1}{R_3} \right) \\ \frac{1}{C_2} \left( -\frac{1}{R_2} - \frac{1}{R_3} \right) & \frac{1}{C_2} \left( -\frac{1}{R_2} - \frac{1}{R_3} \right) \end{bmatrix} \cdot \begin{bmatrix} V_{C_1} \\ V_{C_2} \end{bmatrix} + \begin{bmatrix} \frac{1}{C_1} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \\ \frac{1}{C_2 R_2} \end{bmatrix} V_s$$

$$\text{OUTPUT} = V_{R_2} = V_s - V_{C_1} - V_{C_2}$$

$$y = [-1 \quad -1] \begin{bmatrix} V_{C_1} \\ V_{C_2} \end{bmatrix} + [1] V_s$$