

6-4

PROBLEM 6.3

(a) FROM Fig 6.26, FOR BALL-SCREW

$$v_n = n \Omega_n \quad n = \frac{\text{RAD/S}}{\text{M/S}} = \text{RAD/M}$$

THEN FORCE ON NUT F_n IS RELATED TO SHAFT TORQUE T_n BY

$$F_n = -\frac{1}{n} T_n$$

AND BALL-SCREW IS A TRANSFORMER

$$\text{WITH: } v_n \cdot F_n = n \Omega_n \left(-\frac{1}{n} T_n\right) = -\Omega_n T_n$$

$$v_n \cdot F_n + \Omega_n T_n = 0$$


Now N : threads/cm

$$\therefore n = 200\pi N \quad \text{RAD/M}$$

ADVANCE ONE THREAD

WITH ROTATION OF 2π RAD

$$1 \text{ cm} = .01 \text{ m}$$

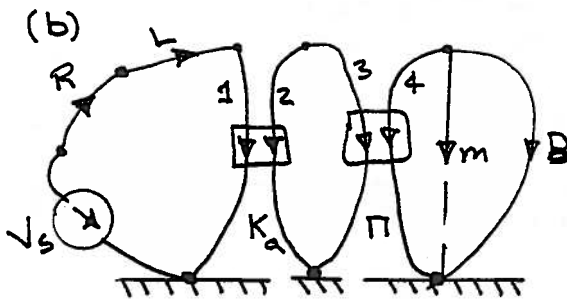

LINEAR GRAPH

STATE VAR

$$v_m, i_L$$

FOR DC MOTOR:

$$v_1 = K_a \Omega_2$$

$$i_1 = -1/K_a T_2$$

FOR BALL-SCREW:

$$F_4 = -\frac{1}{n} T_3$$

$$v_4 = n \Omega_3$$

PROBLEM 6.3 CONTINUED

$$\frac{di_L}{dt} = \frac{1}{L} V_L$$

$$\frac{dv_m}{dt} = \frac{1}{m} F_m$$

$$F_B = B V_B$$

$$V_R = R i_R$$

$$F_4 = -\frac{1}{n} T_3$$

$$\Omega_3 = \frac{1}{n} V_4$$

$$T_2 = -K_a i_1$$

$$V_1 = K_a \Omega_2$$

$$V_L = V_s - V_R - V_1$$

$$F_m = -F_B - F_4$$

$$V_B = v_m$$

$$i_R = i_L$$

$$T_3 = -T_2$$

$$V_4 = v_m$$

$$i_1 = i_L$$

$$\Omega_2 = \Omega_3$$


$$\frac{di_L}{dt} = \frac{1}{L} \left[V_s - R i_L - K_a \left(\frac{1}{n} \right) v_m \right]$$

$$\frac{dv_m}{dt} = \frac{1}{m} \left[-B v_m + \frac{K_a}{n} i_L \right]$$

$$\frac{d}{dt} \begin{bmatrix} i_L \\ v_m \end{bmatrix} = \begin{bmatrix} -R/L & -K_a/nL \\ K_a/nm & -B/m \end{bmatrix} \cdot \begin{bmatrix} i_L \\ v_m \end{bmatrix} + \begin{bmatrix} 1/L \\ 0 \end{bmatrix} V_s$$

PROBLEM 6.7

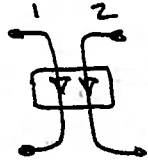
(a) FOR MODEL USE A CONSISTENT dc MOTOR REPRESENTATION WITH $P_1 + P_2 = 0$




$$v_1 = K_a \Omega_2$$

$$i_1 = -1/K_a T_2$$

THE LINEAR GRAPH

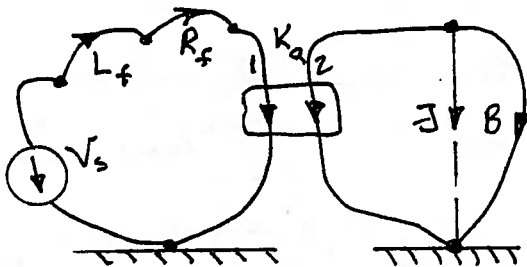

NORMAL TREE

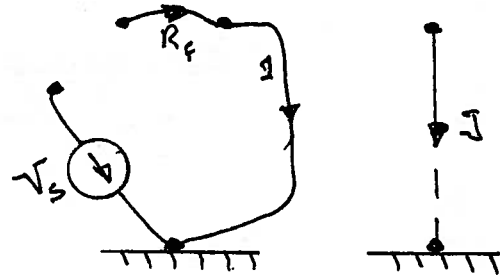

$$(b) \frac{d\Omega_J}{dt} = \frac{1}{J} T_J$$

$$\frac{di_L}{dt} = \frac{1}{L_f} V_L$$

$$T_B = B \Omega_B$$

$$V_R = R_f i_R$$

$$v_1 = K_a \Omega_2$$

$$T_2 = -K_a i_1$$

$$T_J = -T_B - T_2$$

$$V_L = V_s - V_R - v_1$$

$$\Omega_B = \Omega_J$$

$$i_R = i_L$$

$$\Omega_2 = \Omega_J$$

$$i_1 = i_L$$

$$\frac{d\Omega_J}{dt} = \frac{1}{J} [-B \Omega_J + K_a i_L]$$

$$\frac{di_L}{dt} = \frac{1}{L} [V_s - R_f i_L - K_a \Omega_J]$$

$$\frac{d}{dt} \begin{bmatrix} \Omega_J \\ i_L \end{bmatrix} = \begin{bmatrix} -B/J & +K_a/J \\ -K_a/L & -R/L \end{bmatrix} \cdot \begin{bmatrix} \Omega_J \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} V_s$$

PROBLEM 6.7 CONTINUED

(c) MANUF. SPEC. WITH $T^* = K_m i$, $V = K_v \Omega$
 K_m : OZ-IN/AMP K_v : VOLTS/KRPM

FOR $K_m = 6$ OZ-IN/AMP

IN MANUF. CONVENTION $P_1 = P_2$ OR $P_1 - P_2 = 0$

AND $T^* = -T$ AND SO

$$K_v = \frac{\Omega}{V} = K_a$$

$$K_m = \frac{T^*}{i} = \frac{-T}{i} = -(-K_a) = K_a$$

DETERMINE K_a IN SI UNITS

$$K_a: \text{N-m/AMP} : 6 \text{ OZ-IN/AMP} \cdot \frac{1 \text{ lb}}{16 \text{ oz}} \cdot \frac{4.45 \text{ N}}{1 \text{ lb}} \cdot \frac{1 \text{ ft}}{12 \text{ in}} \cdot \frac{(3)}{\text{ft}}$$

$$: \left(\frac{6}{16}\right) \left(\frac{4.45}{12}\right) (3) \text{ N-m/AMP}$$

$$K_a = .043 \text{ N-m/AMP}$$

$$\therefore K_a = .043 \text{ V-s/r}$$

$$\text{RAD/S} \cdot \frac{60 \text{ s}}{\text{min}} \cdot \frac{1}{2\pi} \cdot \frac{1}{1000} = \text{KRPM}$$

$$\therefore K_v = \frac{.043}{60/(2\pi \cdot 1000)} \text{ V/KRPM} = 4.5 \text{ VOLTS/KRPM}$$

(d) WITH CONSTANT CURRENT $i_L = 1$ AMP

$$(i) \frac{d\Omega}{dt} = 0 \quad \therefore B\Omega_T = K_a i_L \quad \text{AND} \quad B = \frac{.043 (1)}{1000 \cdot 2\pi/60}$$

$$\text{OR} \quad B = 0.41 \cdot 10^{-3} \text{ N-m-s}$$

$$(ii) V_T = R i + K_a \Omega = 3 + .043 \left(\frac{1000 \cdot 2\pi}{60} \right) = 3 + 4.5 \text{ V} = 7.5 \text{ V}$$

$$(iii) \text{ Total Power} = P_T = V_T \cdot i = 7.5 \text{ W} : \text{RESISTOR, DAMPER}$$

$$\text{ELECT: } R i^2 = 3 \text{ W}$$

$$\text{MECH: } B\Omega^2 = 0.41 \left(\frac{1000 \cdot 2\pi}{60} \right)^2 \cdot 10^{-3}$$

$$\% P_E = 40\%$$


$$\% P_M = 60\%$$

$$= 4.492 \frac{\text{N-m}}{\text{s}} = 4.5 \text{ W}$$

6-12

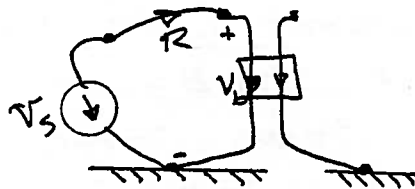PROBLEM 6.8

WITH DC MOTOR AT CONSTANT CONDITIONS
INPUT CIRCUIT IS



$$V_s = iR + V_b$$

AND
$$i = \frac{V_s - V_b}{R} \quad \text{WITH } V_b = K_a \Omega$$

NOW WHEN MOTOR STALLS $\Omega = 0$
 $\therefore V_b = 0$ AND $i = V_s/R$ AND IS A
MAXIMUM. HEAT DISSIPATED IN R
IS ALSO A MAX WITH $\Omega = 0$ AND IS
 $i^2 R$

USING MOTOR DATA FROM PROBLEM 6.7
 $i = V_s/R = 15/3 = 5A$ AND POWER DISSIPATED
IN RESISTOR R IS: $P = 5^2 \cdot 3 = 75W$

REFERING TO PROBLEM 6.7 AT $\Omega = 1000 \text{ rpm}$
AND $V_s = 7.5V$, POWER DISSIPATED IN
 $R = 3W$

PROBLEM 6.9

(a) FOR COIL, EACH TURN HAS LENGTH $2\pi r$ AND FORCE F_T ON EACH TURN IS GENERATED DUE TO CURRENT i IN FIELD B :

$$F_T = -2\pi r B i$$

AND FOR N TURNS, TOTAL FORCE F

$$F = -2\pi r N B i$$

WHERE FROM FIG 6.30 F HAS NEGATIVE (-) SIGN

FOR VOLTAGE V_i IN COIL WITH VELOCITY v


$$V_i = 2\pi r N B v$$

(b) AND RESULTING MODEL IS A TRANSFORMER

$$\begin{bmatrix} V_i \\ i \end{bmatrix} = \begin{bmatrix} K_c & 0 \\ 0 & -1/K_c \end{bmatrix} \begin{bmatrix} v \\ F \end{bmatrix}$$

$$K_c = 2\pi r N B$$

(c)

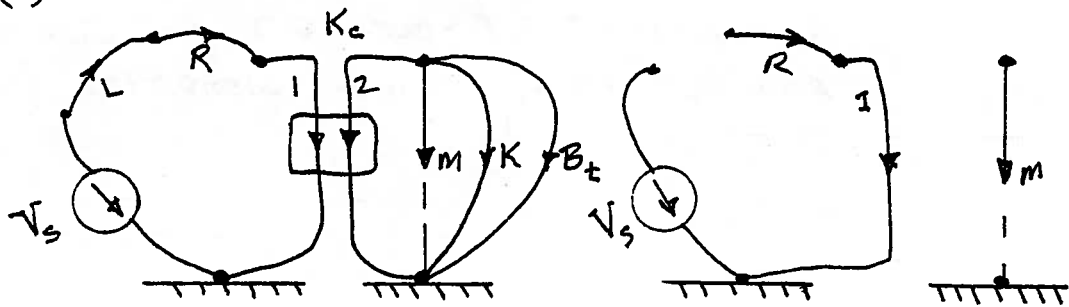

LINEAR GRAPH

NORMAL TREE

STATE VAR. : v_m, i_L, F_K

6-14

PROBLEM 6.9 CONTINUED

$$(d) \quad \frac{dv_m}{dt} = \frac{1}{m} F_m$$

$$\frac{di_L}{dt} = \frac{1}{L} v_L$$

$$\frac{dF_K}{dt} = K v_K$$

$$F_B = B v_B$$

$$v_R = R i_R$$

$$F_2 = -K_c i_1$$

$$v_1 = K_c v_2$$

$$F_m = -F_2 - F_K - F_B$$

$$v_L = v_s - v_R - v_1$$

$$v_K = v_m$$

$$v_B = v_m$$

$$i_R = i_L$$

$$i_1 = i_L$$

$$v_2 = v_m$$


$$\frac{d}{dt} \begin{bmatrix} v_m \\ i_L \\ F_K \end{bmatrix} = \begin{bmatrix} -B/m & K_c/m & -1/m \\ -K_c/L & -R/L & 0 \\ K & 0 & 0 \end{bmatrix} \begin{bmatrix} v_m \\ i_L \\ F_K \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \\ 0 \end{bmatrix} v_s$$

OUTPUT = v_m

$$v_m = \begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_m \\ i_L \\ F_K \end{bmatrix}$$

PROBLEM 6.12

(a)

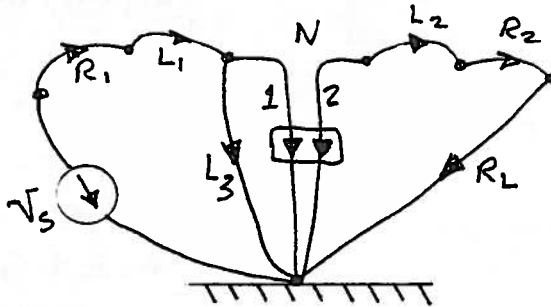

$$N = N_2 / N_1$$

$$V_2 = N V_1$$

$$i_2 = -\frac{1}{N} i_1$$

NOTE: NORMAL TREE
REQUIRES ONE
INDUCTOR, SELECT
 L_3 , It is \therefore
dependent

$$\frac{di_{L1}}{dt} = \frac{1}{L_1} V_{L1}$$

$$\frac{di_{L2}}{dt} = \frac{1}{L_2} V_{L2}$$

$$V_{R1} = R_1 i_{R1}$$

$$V_{R2} = R_2 i_{R2}$$

$$V_{R_L} = R_L i_{R_L}$$

$$V_2 = N V_1$$

$$i_1 = -N i_2$$

$$V_{L3} = L_3 \frac{di_{L3}}{dt}$$

$$V_{L1} = V_s - V_{R1} - V_{L3}$$

$$V_{L2} = V_2 - V_{R2} - V_{R_L}$$

$$i_{R2} = i_{L2}$$

$$i_{R_L} = i_{L2}$$

$$i_{R1} = i_{L1}$$

$$V_1 = V_{L3}$$

$$i_2 = -i_{L2}$$

$$i_{L3} = i_{L1} - i_1$$

$$(1) \frac{di_{L1}}{dt} = \frac{1}{L_1} \left[V_s - R_1 i_{L1} - L_3 \left(\frac{di_{L1}}{dt} - \frac{d}{dt} (+N i_{L2}) \right) \right]$$

$$(2) \frac{di_{L2}}{dt} = \frac{1}{L_2} \left[N L_3 \left(\frac{di_{L1}}{dt} - \frac{d}{dt} (+N i_{L2}) \right) - R_2 i_{L2} - R_L i_{L2} \right]$$

THE STATE EQ MAY BE WRITTEN:

$$(3) \left(1 + \frac{L_3}{L_1} \right) \frac{di_{L1}}{dt} - \left(\frac{L_3 N}{L_1} \right) \frac{di_{L2}}{dt} = \left(-\frac{R_1}{L_1} \right) i_{L1} + \frac{1}{L_1} V_s$$

$$(4) \left(-\frac{N L_3}{L_2} \right) \frac{di_{L1}}{dt} + \left(1 + \frac{N^2 L_3}{L_2} \right) \frac{di_{L2}}{dt} = -\left(\frac{R_2 + R_L}{L_2} \right) i_{L2}$$

6-18

PROBLEM 6.12 CONTINUED

AND PLACED IN A FORM TO SOLVE USING
CRAMER'S RULE

$$\begin{bmatrix} \left(1 + \frac{L_3}{L_1}\right) & -\frac{L_3 N}{L_1} \\ -\frac{N L_3}{L_2} & \left(1 + \frac{N^2 L_3}{L_2}\right) \end{bmatrix} \begin{bmatrix} \frac{d\dot{i}_{L_1}}{dt} \\ \frac{d\dot{i}_{L_2}}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R_1}{L_1} \dot{i}_{L_1} + \frac{V_s}{L_1} \\ -\frac{(R_2 + R_L)}{L_2} \dot{i}_{L_2} \end{bmatrix}$$

$$\text{LET } D = \left(1 + \frac{L_3}{L_1}\right) \left(1 + \frac{N^2 L_3}{L_2}\right) - \frac{N^2 L_3^2}{L_1 L_2} = 1 + \frac{L_3}{L_1} + \frac{N^2 L_3}{L_2}$$

THEN:

$$\frac{d\dot{i}_{L_1}}{dt} = \frac{1}{D} \left[\left(1 + \frac{N^2 L_3}{L_2}\right) \left(-\frac{R_1}{L_1} \dot{i}_{L_1} + \frac{V_s}{L_1}\right) - \frac{L_3 N}{L_1} \frac{(R_2 + R_L)}{L_2} \dot{i}_{L_2} \right]$$

$$\frac{d\dot{i}_{L_2}}{dt} = \frac{1}{D} \left[-\left(1 + \frac{L_3}{L_1}\right) \frac{(R_2 + R_L)}{L_2} \dot{i}_{L_2} + \frac{N L_3}{L_2} \left(-\frac{R_1}{L_1} \dot{i}_{L_1} + \frac{V_s}{L_1}\right) \right]$$

$$\text{AND} \quad \frac{d}{dt} \begin{bmatrix} \dot{i}_{L_1} \\ \dot{i}_{L_2} \end{bmatrix} = \begin{bmatrix} -\frac{R_1}{D L_1} \left(1 + \frac{N^2 L_3}{L_2}\right) & -\frac{L_3 N}{L_1 D L_2} (R_2 + R_L) \\ -\frac{N L_3 R_1}{L_1 L_2 D} & -\frac{(R_2 + R_L)}{L_2 D} \left(1 + \frac{L_3}{L_1}\right) \end{bmatrix} \begin{bmatrix} \dot{i}_{L_1} \\ \dot{i}_{L_2} \end{bmatrix} + \begin{bmatrix} \frac{1}{D L_1} \left(1 + \frac{N^2 L_3}{L_2}\right) \\ \frac{N L_3}{D L_2 L_1} \end{bmatrix} V_s$$

(b) WITH $V_s = \text{CONSTANT}$, THEN \dot{i}_{L_1} & \dot{i}_{L_2} & \dot{i}_{L_3}
ARE ALSO CONSTANTS: REFER TO EQ 3 & 4
WHEN STATE VAR ARE CONSTANT, THEN

$$\dot{i}_{L_1} = V_s / R_1 \quad \dot{i}_{L_2} = 0$$

$$\text{SINCE } \frac{d}{dt} \dot{i}_{L_1} = \frac{d}{dt} \dot{i}_{L_2} = \frac{d}{dt} \dot{i}_{L_3} = 0$$

AND WITH $\dot{i}_{L_2} = 0$ $i_{R_L} = 0$ AND $V_{R_L} = 0$

THUS WITH CONSTANT INPUT, MODEL YIELDS

0 FOR OUTPUT - i.e. $V_{R_L} = 0$